 


## Assessment: Junior FPGA Design Engineer


Hello,  
Greetings of the day!



### UART Packetizer with FSM and FIFO Integration

**Question 1:** Design a digital system which accepts parallel data packets and transmits them serially over a UART-like interface. The digital logic design of the system shall include the RTL development of the following modules.

 1. A Packetizer FSM.
2. An asynchronous FIFO buffer.
3. A UART-like serial output block.
4. A top module interconnecting the above three modules.



### **System Description:**

This module receives 8-bit data words from an external data source and stores them in a FIFO. An FSM reads from this FIFO and generates a serial stream with a custom protocol as described below.

### **Functional Requirements:**

- Data width: 8 bits.
- Baud Rate: Parameterizable (e.g., 9600, 115200).
- Start bit: 1 (logic low).
- Stop bit: 1 (logic high).
- No parity or flow control

### **Inputs:**

- **clk**: System clock (50 MHz)
- **rst**: Active-high synchronous reset
- **data\_in[7:0]**: Incoming data byte
- **data\_valid**: Pulse when new data is valid
- **tx\_ready**: Indicates external receiver is ready i.e., to simulate handshaking.

### **Outputs:**

- **serial\_out**: Serial output line
- **fifo\_full**: High when FIFO is full
- **tx\_busy**: High while transmission is in progress

## Module level requirements:

### 1. **FIFO Buffer:**

- Depth: 16.
- Asynchronous or synchronous FIFO.
- Provide fifo\_full, fifo\_empty, and data\_out\_valid signals.

### 2. **FSM Logic steps:**

- Detects when FIFO non-empty.
- Waits for tx\_ready signal.
- Reads FIFO.
- Transmits 10-bit packet via serial\_out bit by bit.
- Returns to IDLE when done.

Considering the above description, provide the following.

- a) Design **VHDL/Verilog RTL code** for the modules.
- b) Develop a **simulation testbench** and provide the following **results**.
  - 1. FIFO **write** and **read**.
  - 2. Serial **output waveform** along with **fifo\_full** and **tx\_busy** signals.
  - 3. At least **2 valid packets** with proper framing.
  - 4. **FSM state transitions**.
- c) Generate documentation with following details
  - 1. **FSM state diagram** along with state transitions.
  - 2. **FIFO usage explanation**.
  - 3. **Rational for synchronous/asynchronous FIFO**.

## **Question 2**

- a) Carry **out synthesis**, place and route on AMD-Xilinx Vivado tool with a target **FPGA** from chosen from Kintex/Virtex family of FPGAs?
- b) Provide the **synthesis** and **timing reports** generated by **AMD-Xilinx Vivado tool**.
- c) Report the **resource utilization** and **achieved maximum operating clock frequency** at **Synthesis level** and **post-place** and **route level**?

- d) Describe the **encoding technique is used in the FSM implementation**. Provide a **tool generated report** indicating the type of encoding technique used for FSM implementation.
- e) **Propose techniques to increase the maximum operating frequency** of the **RTL** modules developed in question 1.

**Note:**

- **Send the response as a zip file with clear instructions on how to open the file.**
- Assume necessary parameters for implementing the above RTL modules and list the assumptions at the relevant sections.
- Well-structured and clean RTL code will earn brownie points.
- Open-source RTL modules shall not be utilized and strongly discouraged.
- Avoid generic answers.
- Provide the response within five pages, excluding the source code and support files.